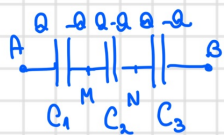


Gruparea în serie a condensatoarelor:



$$C_{AB} = C_{es} = ?$$

$$C = \frac{Q}{U_{12}} = \frac{Q}{V_1 - V_2}$$

$$\left. \begin{aligned} C_1 = C_{AM} &= \frac{Q}{V_A - V_M} \Rightarrow V_A - V_M = \frac{Q}{C_1} \\ C_2 = C_{MN} &= \frac{Q}{V_M - V_N} \Rightarrow V_M - V_N = \frac{Q}{C_2} \\ C_3 = C_{NB} &= \frac{Q}{V_N - V_B} \Rightarrow V_N - V_B = \frac{Q}{C_3} \end{aligned} \right\} \xrightarrow{(*)} V_A - V_B = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$\Downarrow$

$$C_{es} = \frac{Q}{V_A - V_B} = \frac{Q}{Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)} \Rightarrow C_{es} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} \approx R_{ep}$$

$$C_{AB} = C_{es} = \frac{Q}{V_A - V_B}$$

Gruparea în paralel a condensatoarelor:



$$C_{AB} = C_p = ? \quad (C_{AB} = C_e = \frac{Q}{V_A - V_B})$$

$$\left. \begin{aligned} C_1 &= \frac{Q_1}{V_A - V_B} \Rightarrow Q_1 = C_1 (V_A - V_B) \\ C_2 &= \frac{Q_2}{V_A - V_B} \Rightarrow Q_2 = C_2 (V_A - V_B) \\ C_3 &= \frac{Q_3}{V_A - V_B} \Rightarrow Q_3 = C_3 (V_A - V_B) \end{aligned} \right\} \xrightarrow{(*)} \begin{aligned} Q_1 + Q_2 + Q_3 &= (V_A - V_B)(C_1 + C_2 + C_3) \\ Q &= Q_1 + Q_2 + Q_3 \end{aligned}$$

$$C_p = \frac{Q}{V_A - V_B} = \frac{(V_A - V_B)(C_1 + C_2 + C_3)}{(V_A - V_B)} \Rightarrow C_p = C_1 + C_2 + C_3$$

$$W_{el} = \frac{1}{2} \cdot \sum_{i=1}^{\infty} Q_i \cdot V_i$$

$$W_{el} = \begin{cases} \frac{1}{2} Q \cdot U_{AB} \\ \frac{1}{2} \cdot \frac{Q^2}{C} \\ \frac{1}{2} \cdot C U_{AB}^2 \end{cases}$$

Prob. examen:

1. $C = 2 \mu F = 2 \cdot 10^{-6} F$

$U = 50 V$

$W_d = ?$

$W_d = \frac{1}{2} \cdot C \cdot U^2 = \frac{1}{2} \cdot 2 \cdot 10^{-6} \cdot 2500 = 2,5 \cdot 10^{-3} J$

1. (Robotica)

$D = 3 \cdot 10^{-2} m$

$d = 2 \cdot 10^{-3} m$

$E = 10^5 V/m$

a) $U = ?$

b) $Q = ?$


$Fd = qE$

a) $U = \frac{L}{2} = \frac{qEd}{2} = Ed = 10^5 \cdot 2 \cdot 10^{-3} = 2 \cdot 10^2 V$

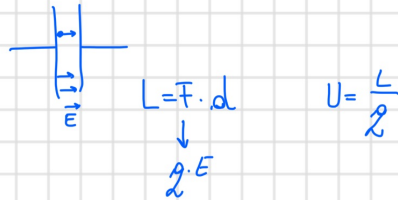b) $R = 1,5 \cdot 10^{-2} m$

$S = \pi R^2 = 225 \cdot 10^{-6} \pi \cdot m^2$

$C = \frac{8,85 \cdot 10^{-12} \cdot 225 \cdot \pi \cdot 10^{-6}}{2 \cdot 10^{-3}} = \dots$



$$\boxed{\begin{aligned} C &= \frac{Q}{L} = \frac{\epsilon_0 \cdot S}{d} \\ U &= \frac{L}{q} \\ L &= Fd = qE \end{aligned}}$$

21/863

$C_1 = 6 \mu F$

$C_2 = 10 \mu F$

$C_3 = 16 \mu F$

$C_{ep} = ? = C_1 + C_2 + C_3 = 32 \cdot 10^{-6} F$

$C_{es} = ? = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = \frac{C_1 C_2 C_3}{C_2 C_3 + C_1 C_3 + C_1 C_2} = \frac{10 \cdot 16 \cdot 6}{160 + 96 + 60}$

$= \frac{10 \cdot 16 \cdot 6}{316} = \frac{240}{79} \mu F$

23/863

$$C = 50 \mu F$$

$$C_1 = 75 \mu F$$

$C_2 = ?$ e în paralel sau în serie?

$$50 = \frac{1}{\frac{1}{75} + \frac{1}{C_2}} \Rightarrow 50 = \frac{75C_2}{C_2 + 75} \Rightarrow 50C_2 + 3750 = 75C_2$$

$$\Rightarrow 25C_2 = 3750 \quad | : 25$$

$$\Rightarrow 5C_2 = 750$$

$$\Rightarrow C_2 = 150$$

25...

27/863.

$$C_2 = \frac{1}{2} C_1$$

$$U_2 = 2 \cdot U_1$$

$$\frac{W_{el1}}{W_{el2}} = ?$$

$$W_{el} = \begin{cases} \frac{1}{2} Q \cdot U_{AB} \\ \frac{1}{2} \cdot \frac{Q^2}{C} \\ \frac{1}{2} \cdot C U^2 \end{cases}$$

$$W_{el1} = \frac{1}{2} \cdot C_1 \cdot \left(\frac{1}{2} U_2 \right)^2$$

$$W_{el2} = \frac{1}{2} \cdot \frac{1}{2} C_1 \cdot U_2^2 \quad (1)$$

$$\frac{W_{el1}}{W_{el2}} = \frac{1}{2}$$

29/863.

$$D = 2 \cdot 10^{-2} m \Rightarrow R = 10^{-2} m \Rightarrow S = \pi \cdot 10^{-4} m^2$$

$$d = 5 \cdot 10^{-4} m$$

$$U = 200 V$$

a) $W_{el} = ?$

b) $\frac{W_{el}}{V} = ?$

$$C = \frac{\epsilon_0 S}{d} = \frac{8,85 \cdot 10^{-12} \cdot \pi \cdot 10^{-4}}{5 \cdot 10^{-4}} = 177 \pi \cdot 10^{-10} F$$

$$W_{el} = \frac{1}{2} \cdot 4 \cdot 10^4 \cdot 177 \pi \cdot 10^{-10} = 354 \pi \cdot 10^{-10} J$$