
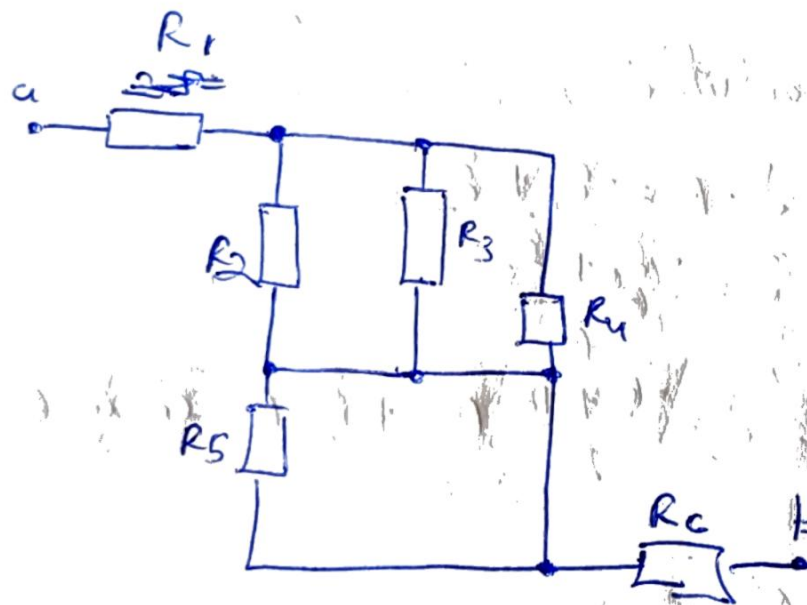


4/1/17

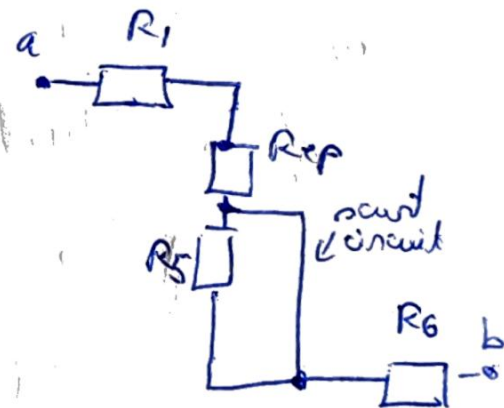

$\Rightarrow$




$$R_{eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{6} + \frac{1}{2} + \frac{1}{4}} = \frac{1}{\frac{6}{12}} = 2 \Omega$$

$$R_{eq} = R_1 + R_{eq} + R_6 = (2 + 2 + 3) \Omega = 7 \Omega$$


(R_{ab})

4/9/15

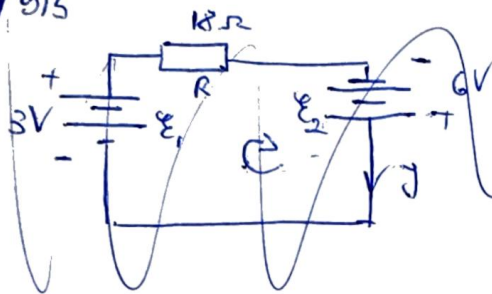

a) $J = ?$, direcția curentului
b) $f(d) = \dots$

5/8/15

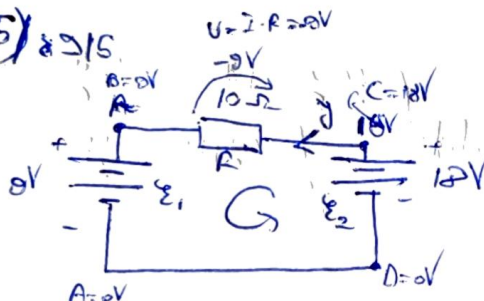

a) $J = ?$, direcția curentului
b) $f(d) = \dots$


a) Se alege un sens arbitrar pentru curent

Leg II Kirchhoff: $J \cdot R = -E_1 + E_2$
 $J = \frac{-E_1 + E_2}{R}$

$J = \frac{-9 + 12}{10} A = +0,3 A$, curent

#

3/8/15

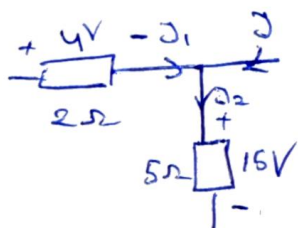

$J = ?$, direcția J

Leg I:

$J_1 = \frac{4V}{2\Omega} = 2A$

$J_2 = \frac{16V}{5\Omega} = 3A$

Leg II: $J_2 = J_1 + J \Rightarrow J = J_2 - J_1 = (3 - 2)A = 1A$
 pe stânga